



STT TELKOM

Modul #05

TE3113

SISTEM KOMUNIKASI 1


RECEIVER FM & AGC:

Superheterodyne, Demodulator FM,

FM Stereo, AGC

Kelas TE-29-02

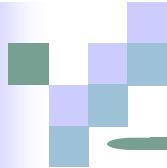
**Program Studi S1 Teknik Telekomunikasi
Departemen Teknik Elektro - Sekolah Tinggi Teknologi Telkom
Bandung – 2007**




FM receiver




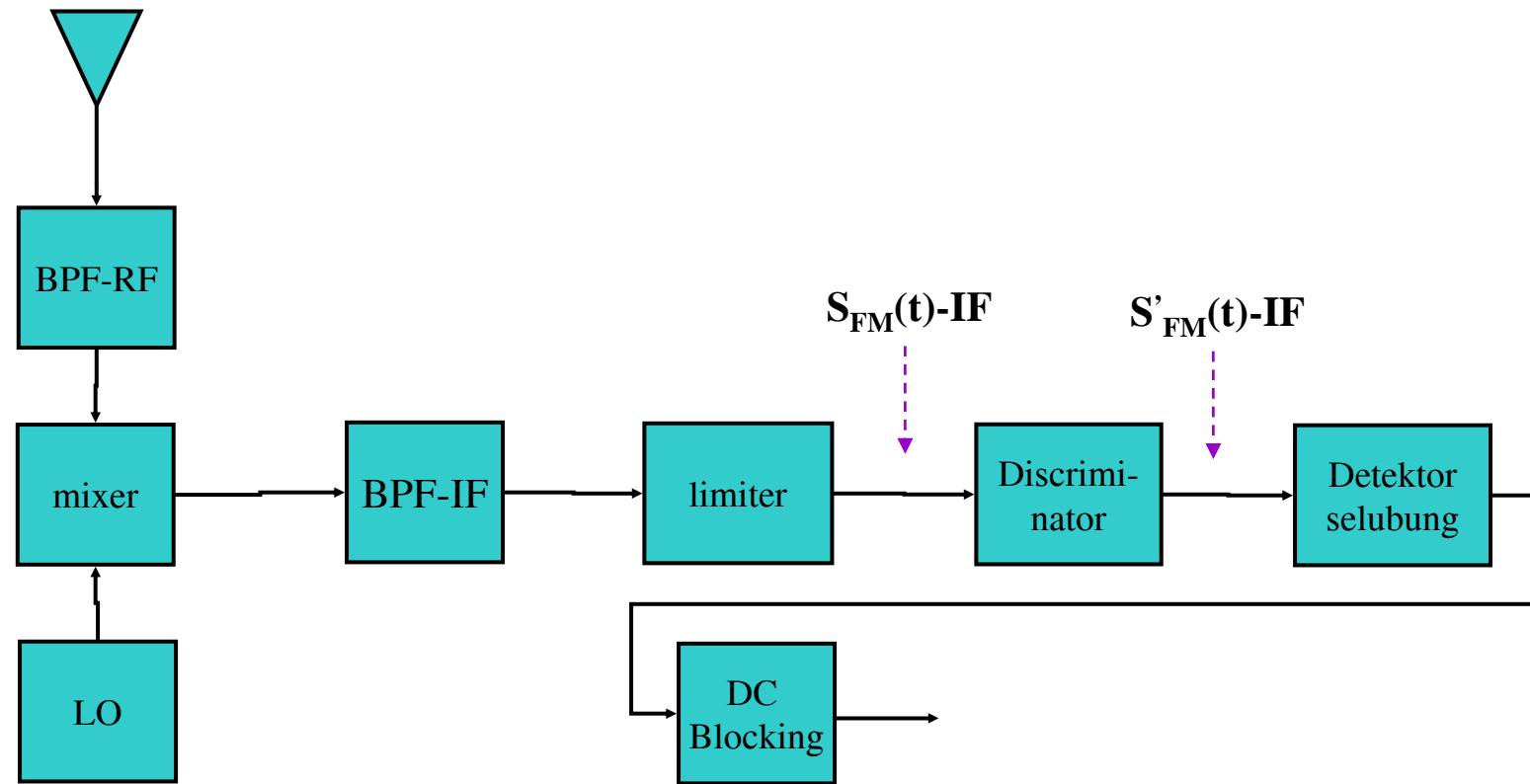
- FM receiver is similar to the superheterodyning (down converting) layout:



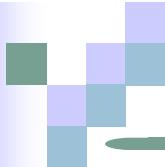



Up Converter (di Pemancar)

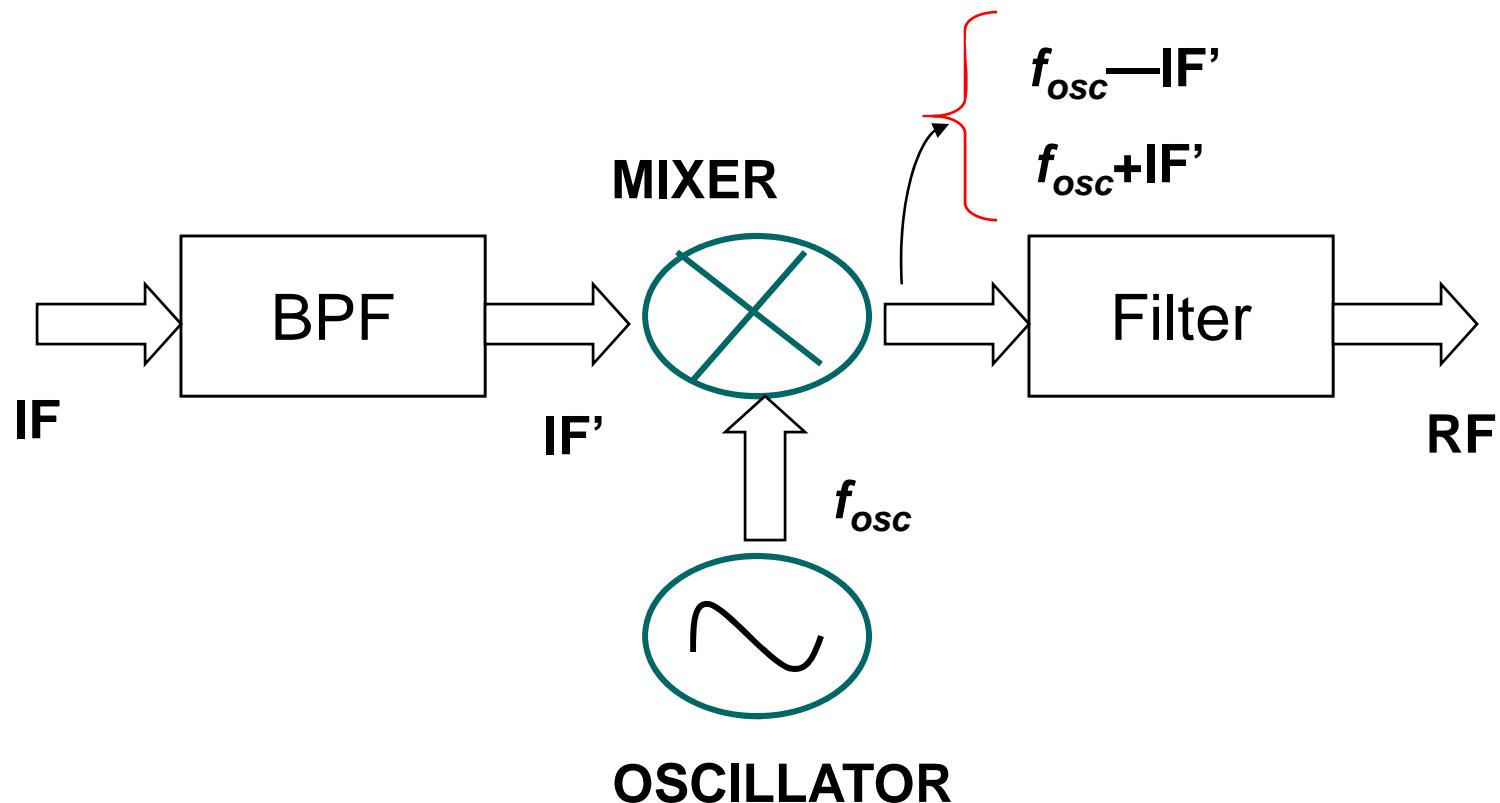

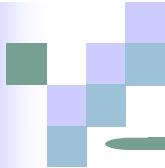

Down Converter (di Penerima)

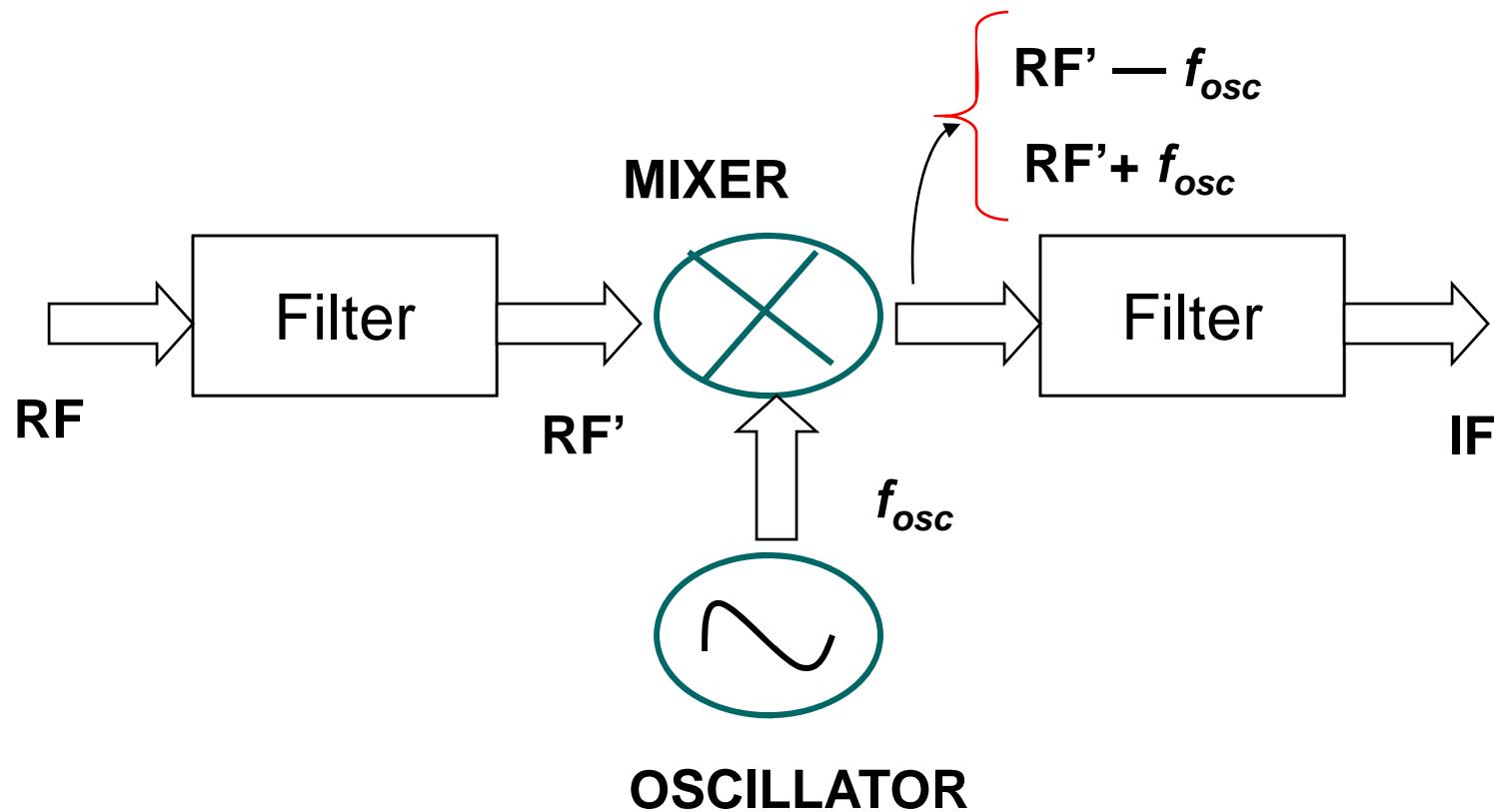

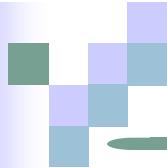


Limiter



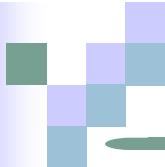- A limiter is a circuit whose output is constant for all input amplitudes above a threshold
- Limiter's function in an FM receiver is to remove unwanted amplitude variations of the FM signal





Demodulasi Sinyal FM



Dengan menggunakan diskriminasi/differensiator


- Pada sinyal FM, informasi terkandung pada frekuensi sinyal FM

$$S_{FM}(t) = A_c \cos \left[2\pi f_{IF} t + 2\pi k_f \int_0^t m(t) dt \right]$$

- Jika dilakukan diferensiasi terhadap $S_{FM}(t)$ (\Rightarrow keluaran discriminator) didapat :


$$S'_{FM}(t) = A_c [2\pi f_{IF} + 2\pi k_f m(t)] \sin \left(2\pi f_{IF} t + 2\pi k_f \int_{-\infty}^t m(t) dt \right)$$

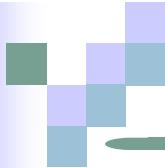Informasi terkandung pada bagian **selubung** dari $S'_{FM}(t)$




Demodulasi Sinyal FM

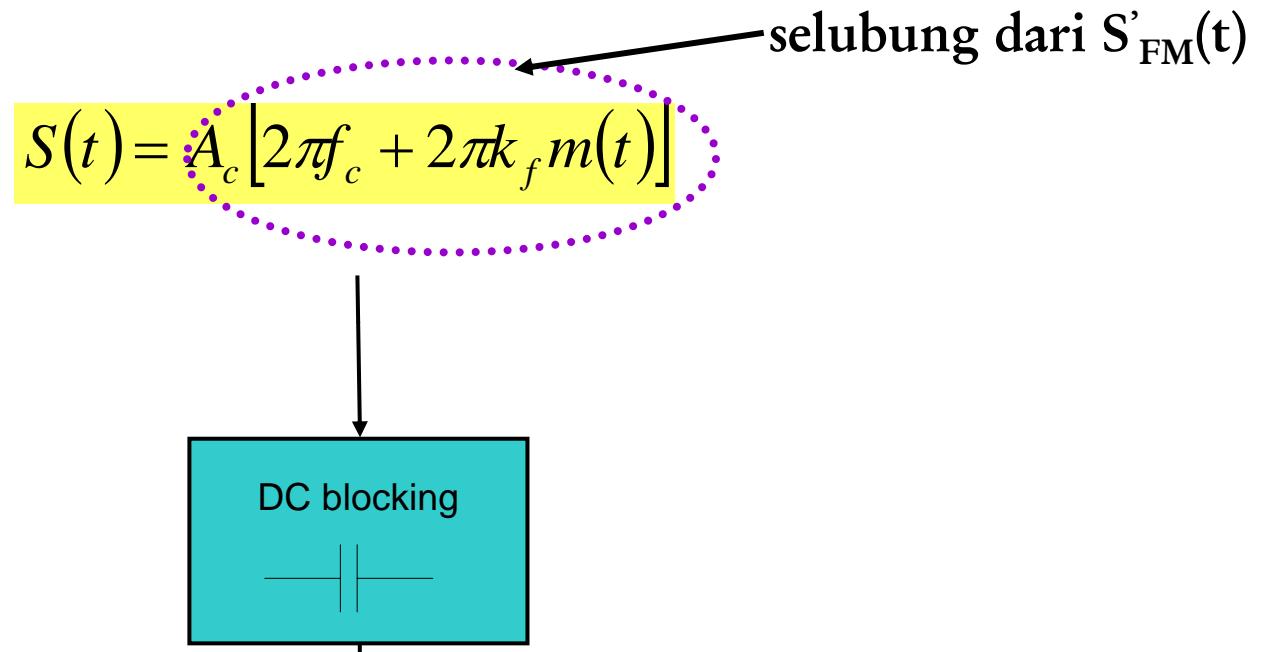- Keluaran detektor selubung (masukan DC blocking):



- Keluaran DC blocking:
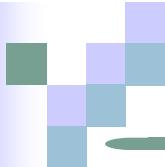
$$\hat{m}(t) = A_c 2\pi k_f m(t) = C \cdot m(t)$$




Discriminator




- The heart of FM is this relationship

$$f_i(t) = f_c + k_f m(t)$$

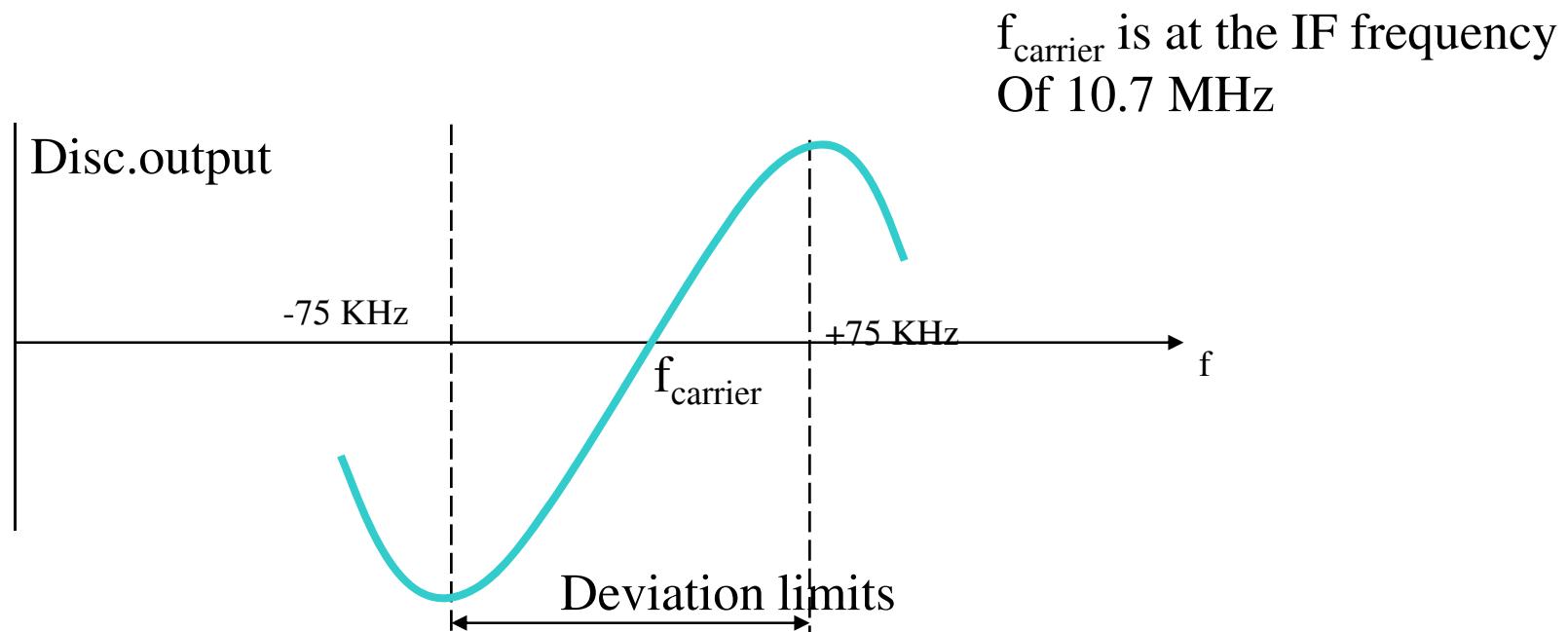- What we need is a device that linearly follows inst. frequency




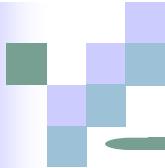


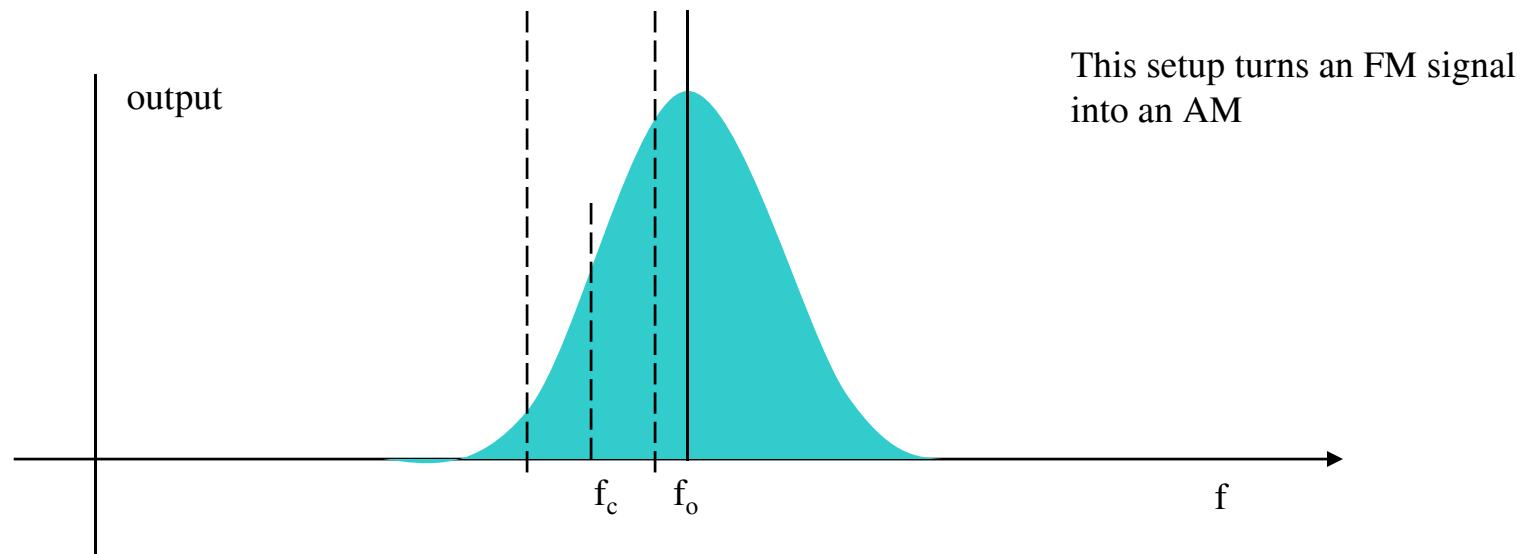Examples of discriminators



- Slope detector - simple LC tank circuit operated at its most linear response curve




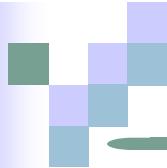

Commercial FM



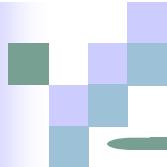
- Commercial FM broadcasting uses the following parameters
 - Baseband: $15\text{KHz} = W = fm$
 - Deviation ratio: 5
 - Peak freq. Deviation = 75KHz
 - ➡ $B_{FM} = 2(\beta+1)W = 2 \times 6 \times 15 = 180\text{KHz}$




Commercial FM spectrum



- The FM landscape looks like this

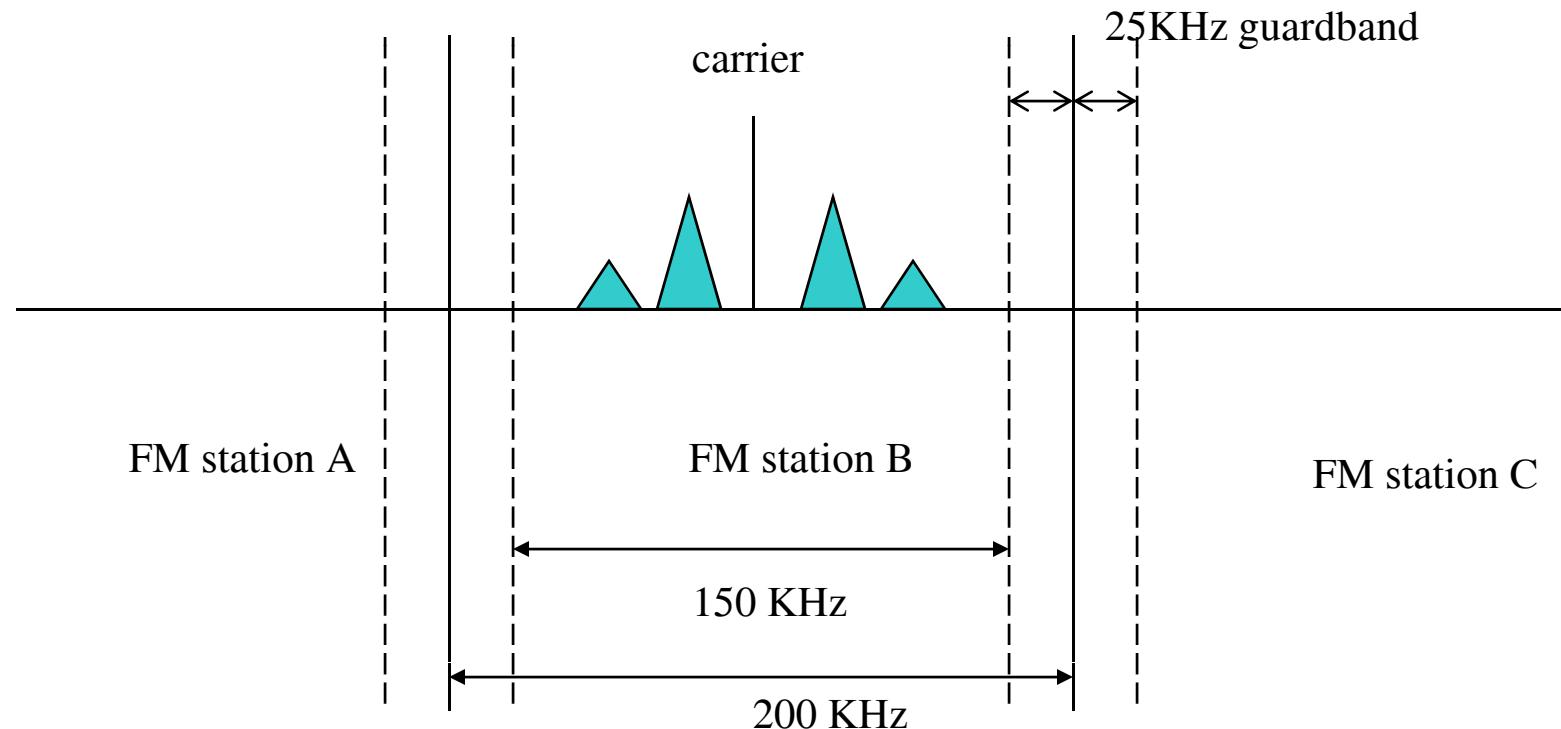

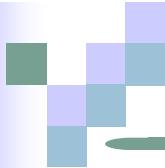



FM stereo:multiplexing



- First, two channels are created; (left+right) and (left-right)
- Left+right is useable by monaural receivers

Left channel

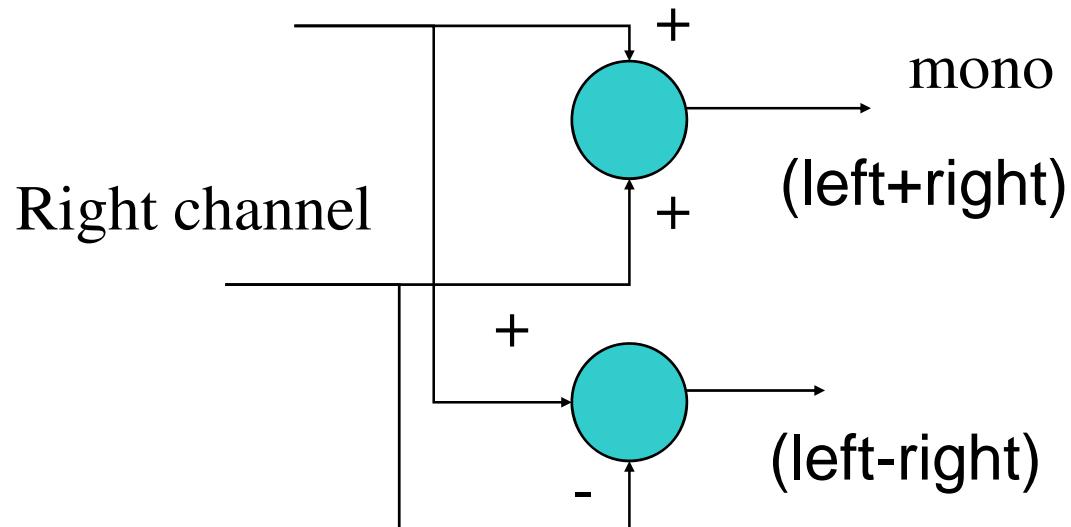


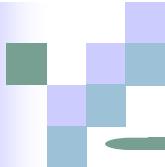


Subcarrier modulation



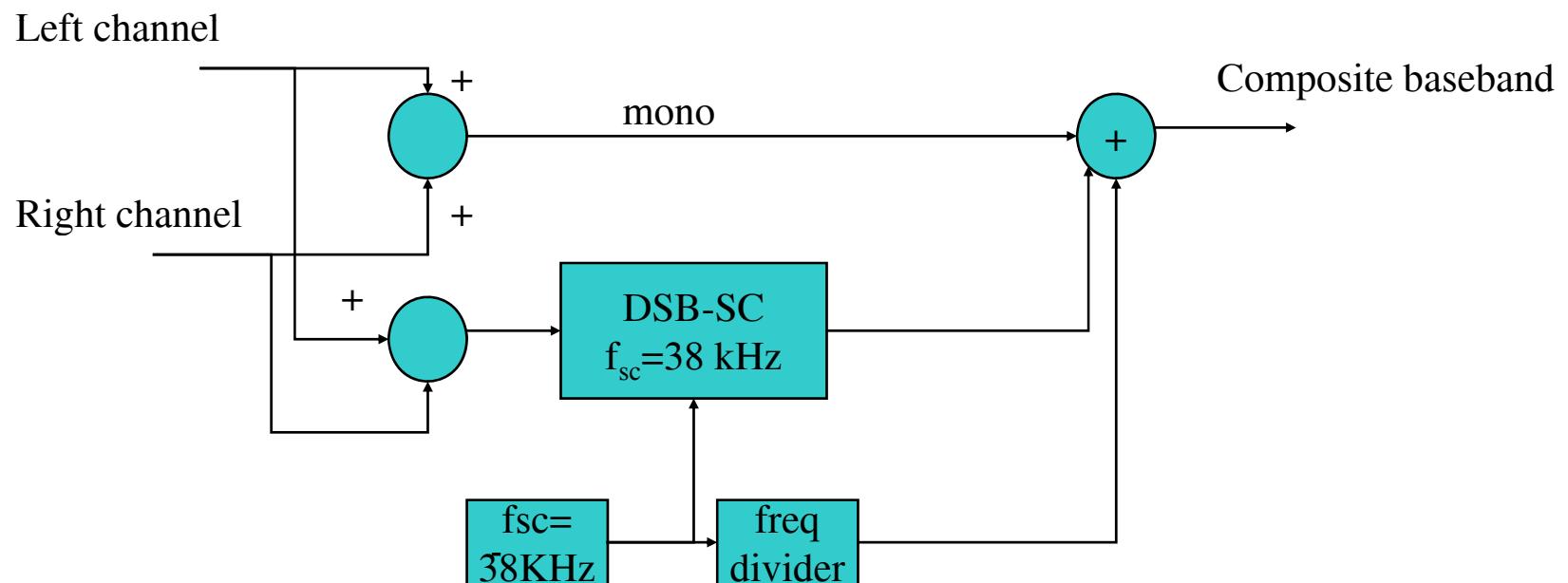- The mono signal is left alone but the difference channel is amplitude modulated with a 38 KHz carrier




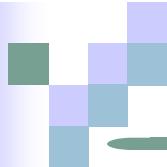


Stereo signal



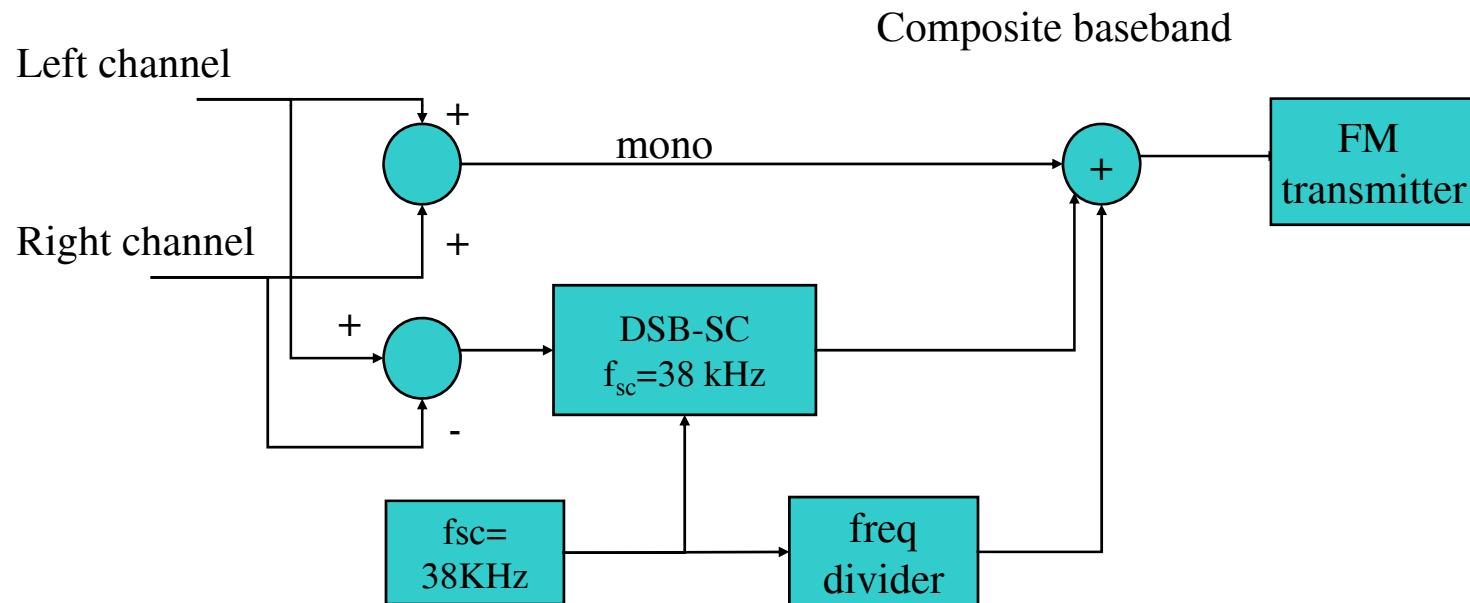- Composite baseband signal is then frequency modulated




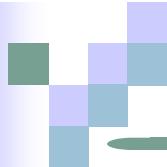


Stereo spectrum



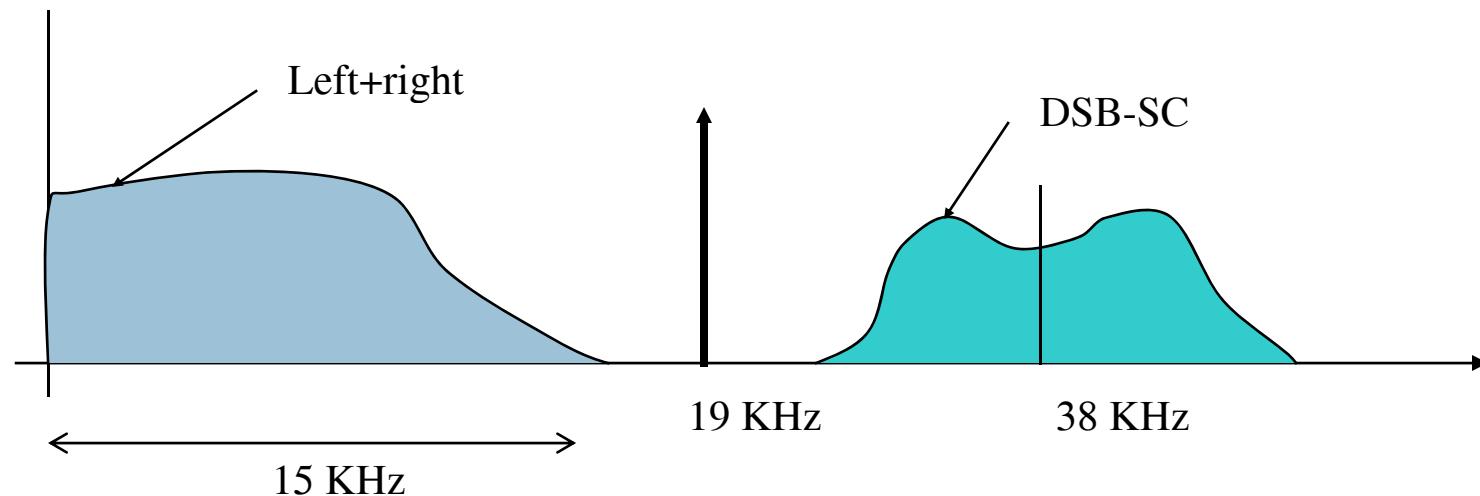- Baseband spectrum holds all the information.
It consists of composite baseband, pilot tone and DSB-SC spectrum




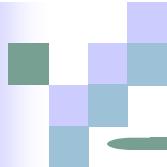


Stereo receiver




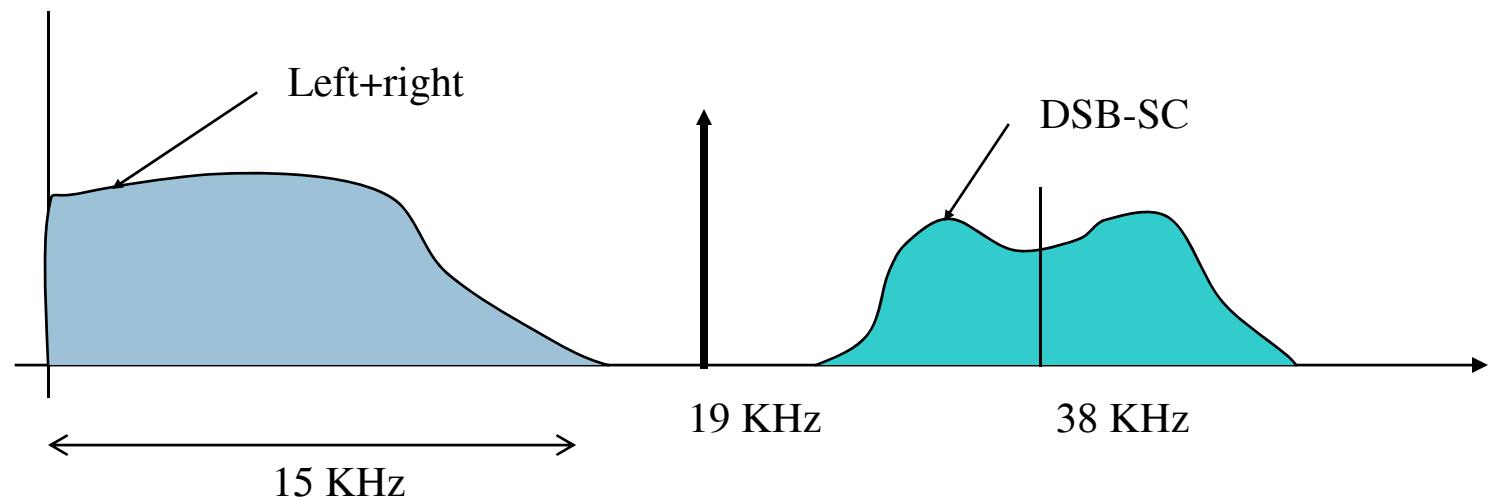
- First, FM is stripped, i.e. demodulated
- Second, composite baseband is lowpass filtered to recover the left+right and in parallel amplitude demodulated to recover the left-right signal




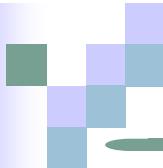



Stereo receiver diagram

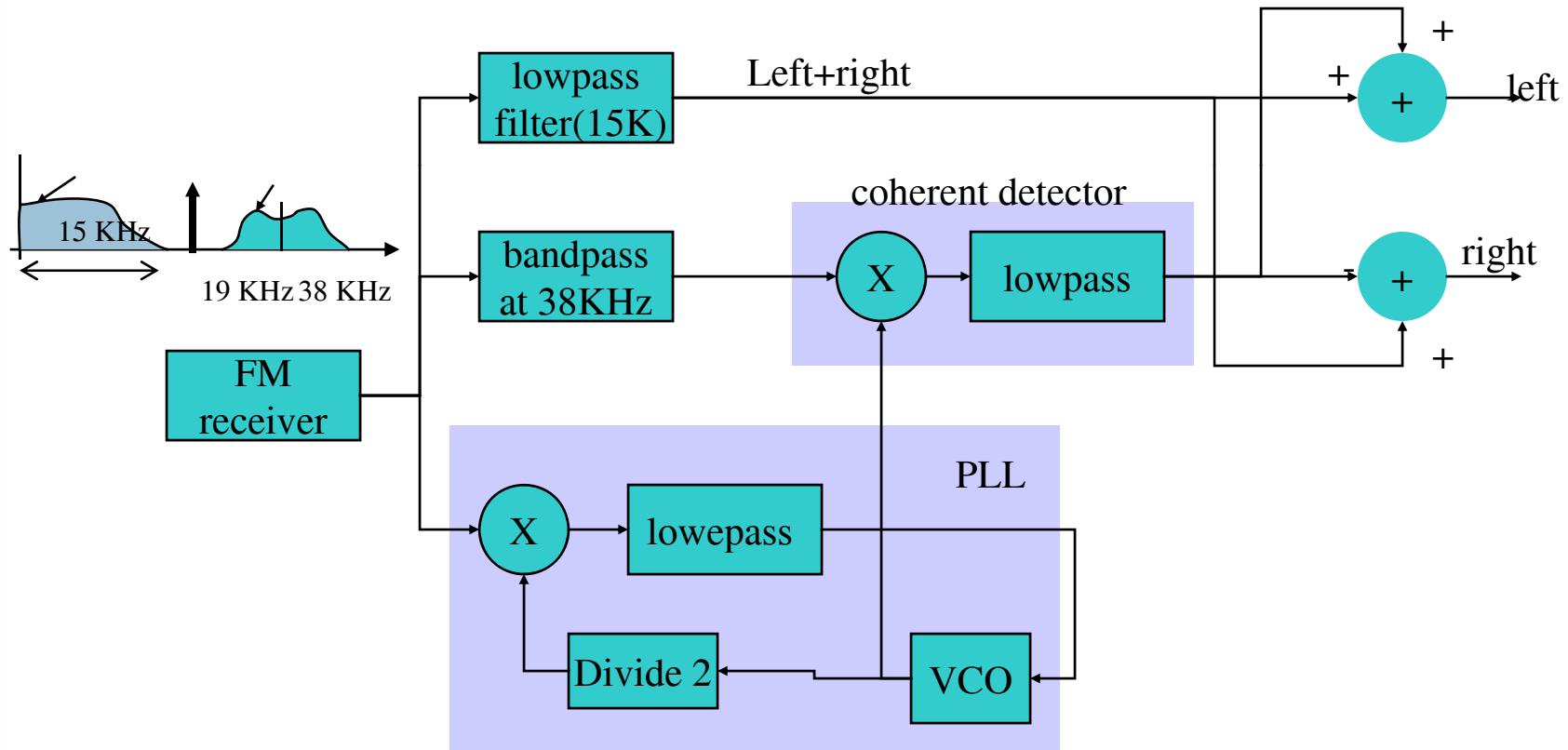

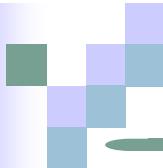



Zero crossing detector

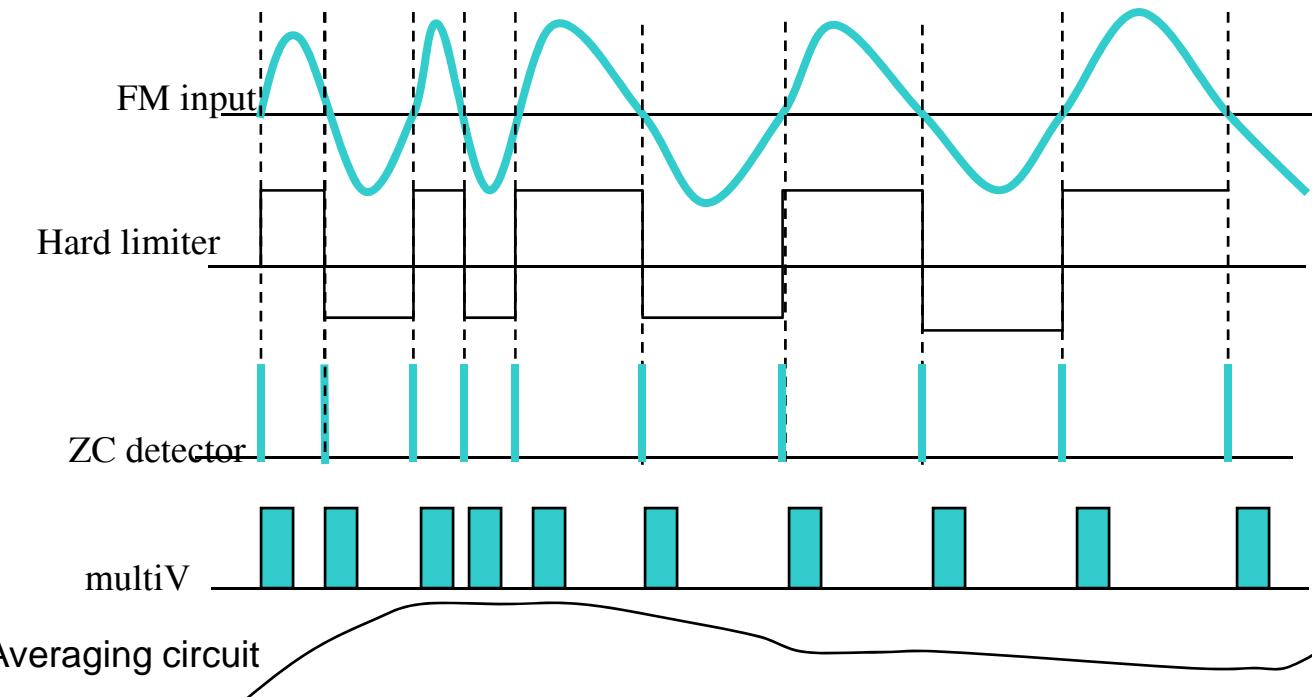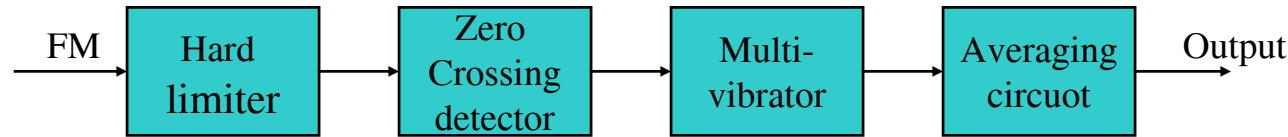

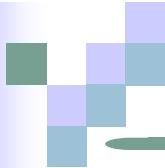

AGC (Automatic Gain Control)

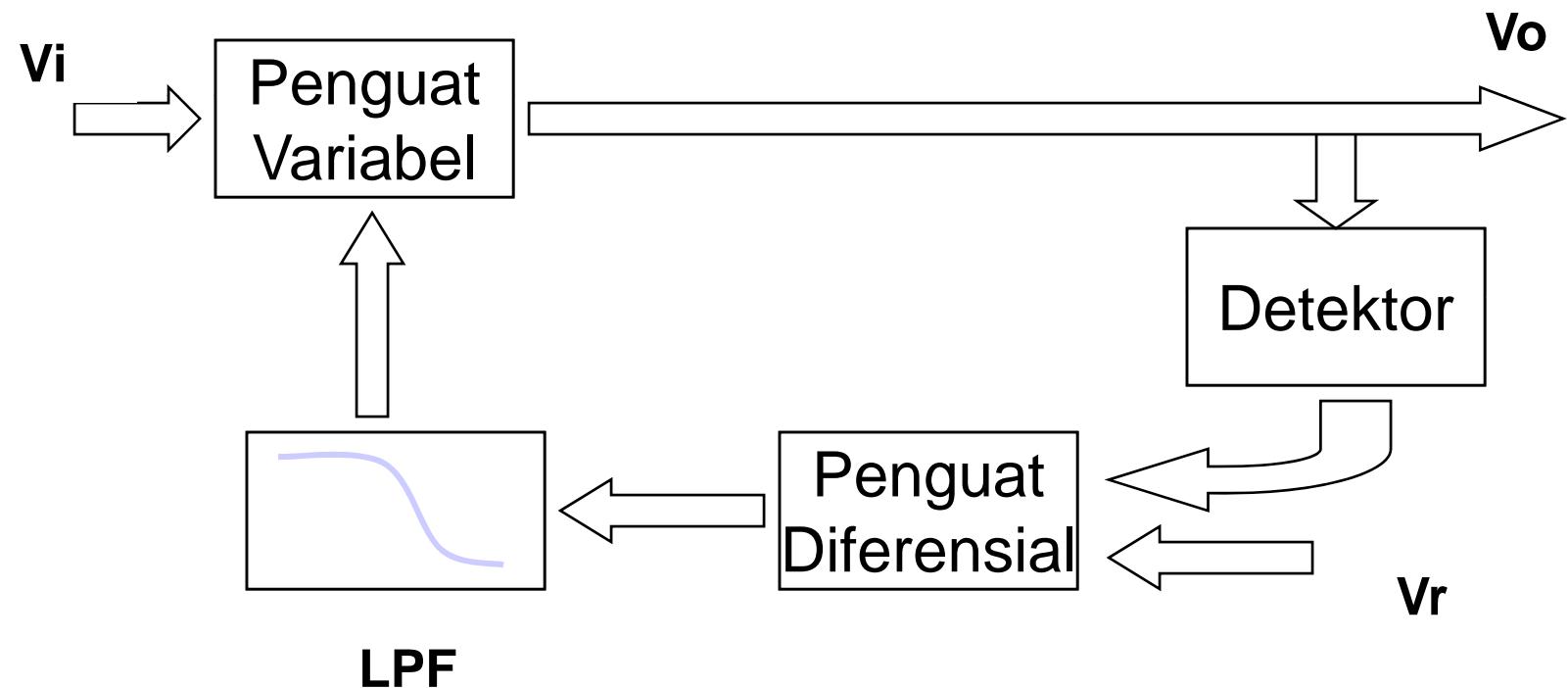

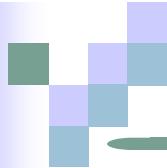

AGC (Automatic Gain Control)

